

HW 1

1. a. Switch
- b. Adding a capacitor makes it useful for timing info
- c. speed, size, power

2.

i. V_{CE}

- x axis

ii. I_C

y axis

iii. V_{BE}

held cst

iv. V_{CE}

swept

v. V_i , V_o

vii.

Cutoff: $|V_{BE}| < |V_{BE(on)}| \rightarrow I_C \approx 0A$

active: $I_C = I_{SE} \left(\frac{V_{BE}}{V_T} \right) \left(1 + \frac{V_{CE}}{V_A} \right)$

ix.

The information in this section tells you how a transistor behaves when you keep V_{BE} cst & sweep V_{CE}

b.

i. V_{DS}

x axis

ii. I_{DS}

y axis

iii. V_{GS}

held cst

iv. V_{DS}

swept

v. V_i , V_o

vii.



$I_{DS} = \frac{k}{2} \frac{W}{L} (V_{GS} - V_{TP})^2 (1 + \lambda \cdot V_{DS})$


ix.

The information in this section tells you how a transistor behaves when you keep V_{GS} cst & sweep V_{DS}

c.

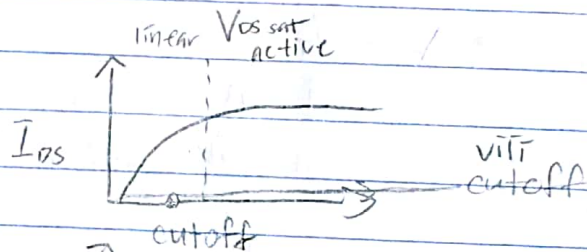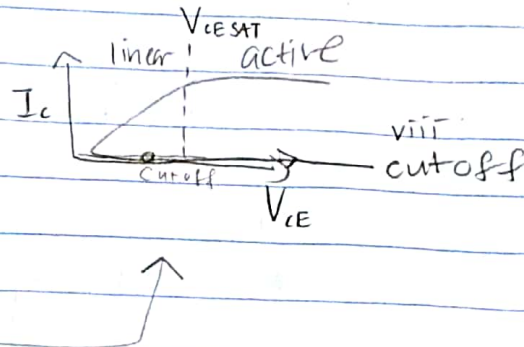If my transistor was biased in the active region, it would be good for knowing what happens when you the input current is too low & goes to cutoff.



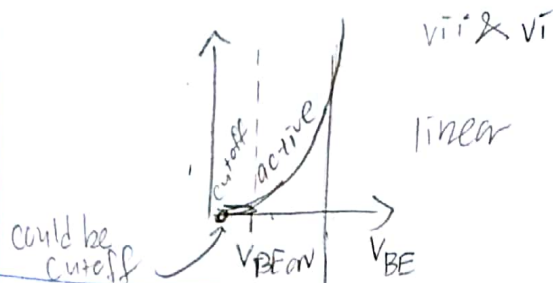

3.

$$V_{CE} = 3V_{CEsat} \leq V_{BE}$$

i.

V_{BE} x axis

ii

$-I_C$ y axis

iii

V_{CE} cst

iv

V_{BE} swept

vii

$$V_{CE} = 3V_{CEsat} > V_{BE} - V_{BE(on)}$$

ix.

The info. in this section tells you how a BJT transistor behaves when you keep V_{CE} cst & sweep V_{BE} .

b.

i

V_{GS} x axis

ii


I_{DS} y axis

iii

V_{DS} cst

iv

V_{GS} swept

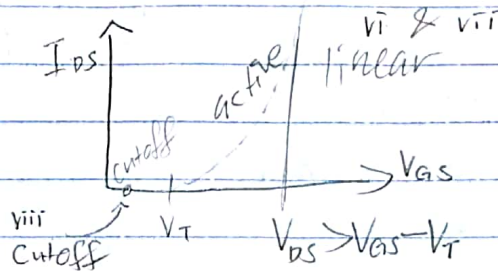

vii.

$$V_{DS} > V_{GS} - V_T$$


ix.

The information in this section tells us how a MOSFET behaves when you keep V_{DS} cst & sweep V_{GS} .

c.

If my transistor was biased in the active region this would be useful when keeping V_{CE} / V_{DS} constant.

4.

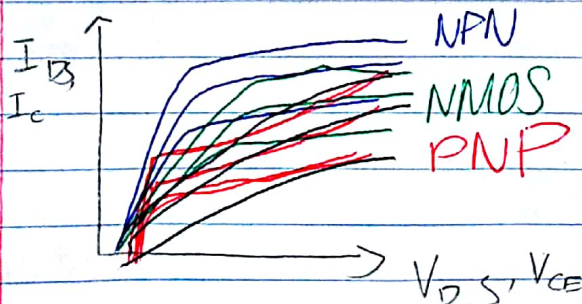

PMOS

b) for NMOS / npr

c) for PMOS / pnp

$I_{DS} & I_C$
positive
 $I_{DS} & I_C$
negative

5. BJTs

a. $I_c = I_s e^{\left(\frac{V_{BE}}{V_T}\right)} \left(1 + \frac{V_{CE}}{V_A}\right)$ active $|V_{CE}| > |V_{CE_SAT}|$
 $I_c \approx 0A$ cut off $|V_{BE}| > |V_{BE_ON}|, A$
 $|V_{BE}| < |V_{BE_ON}|$

b. inputs V_{CE}, V_A, V_{BE}, V_T

c. output I_c

d.

e.

6. Mosfets

a. $I_{DS} = \frac{k'}{2} \frac{W}{L} (V_{GS} - V_{TP})^2 (1 + \lambda V_{DS})$ active
 $|V_{GS}| > |V_T|, |V_{DS}| > |V_{GS} - V_T|$ active
 $I_{DS} \approx 0A$ cutoff

b. inputs V_{GS}, V_{TP}, V_{DS}

c. cut put I_c

d.

e.

7.