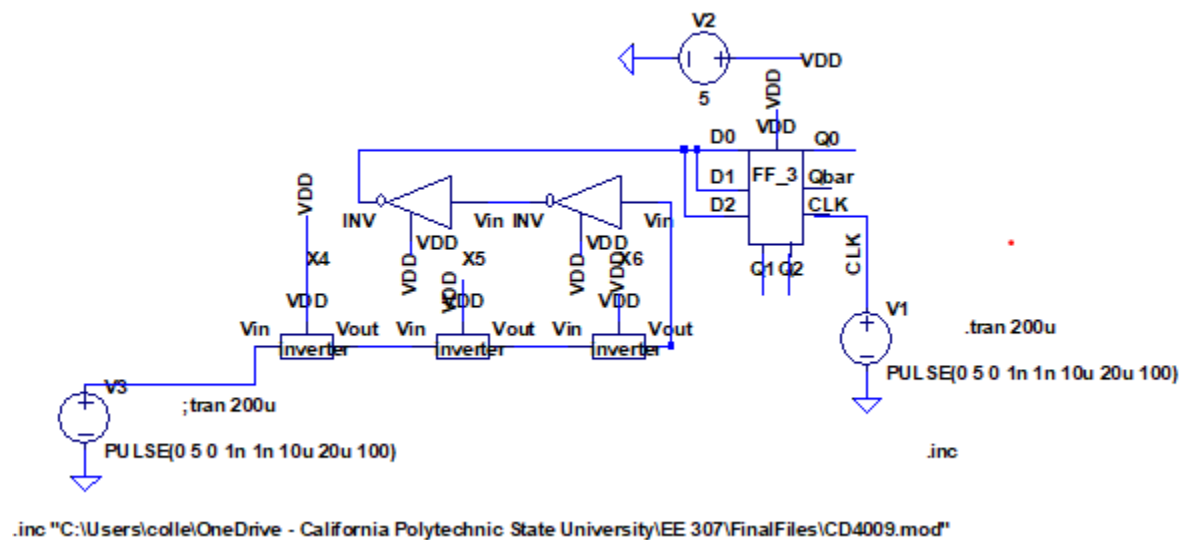



On behalf of our group, we would like to apologize for the timeliness of our homework 8 submission. We appreciate any feedback and commentary for this assignment. We only wish to demonstrate to you that we understand

- the application of D-flip flops to create a multi-address and multi-word register
- the application of AND gates and inverters to create a SRAM memory cell
- the application of NAND gates to create a 2:4 Decoder for the register addresses

and hope to receive any credit if possible. Thank you for your consideration.



Register attempted

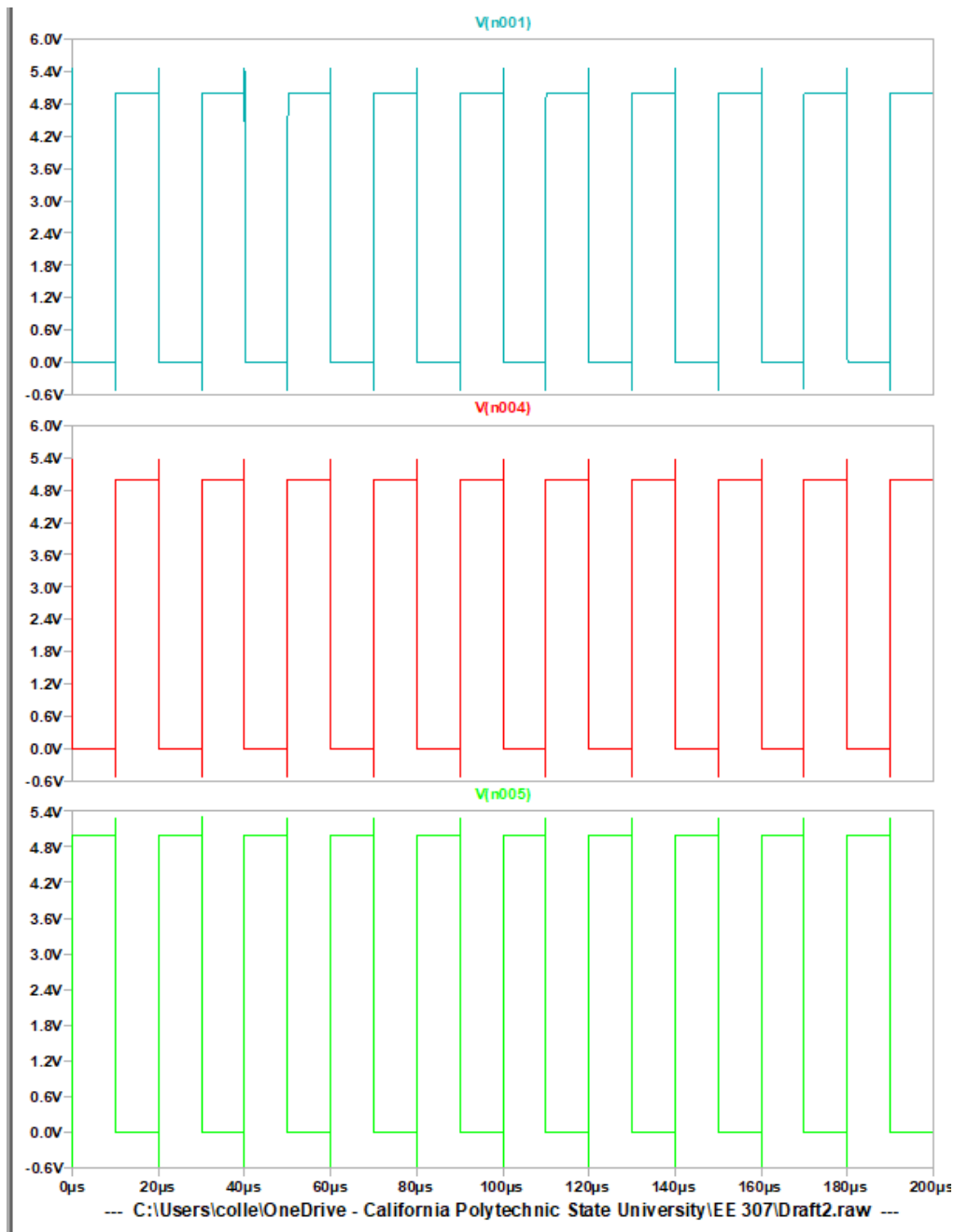

SRAM to register attempted

Colleen Lau  
Tedmon Tran  
EE 307 Smilkstein - HW 8  
March 25, 2018