
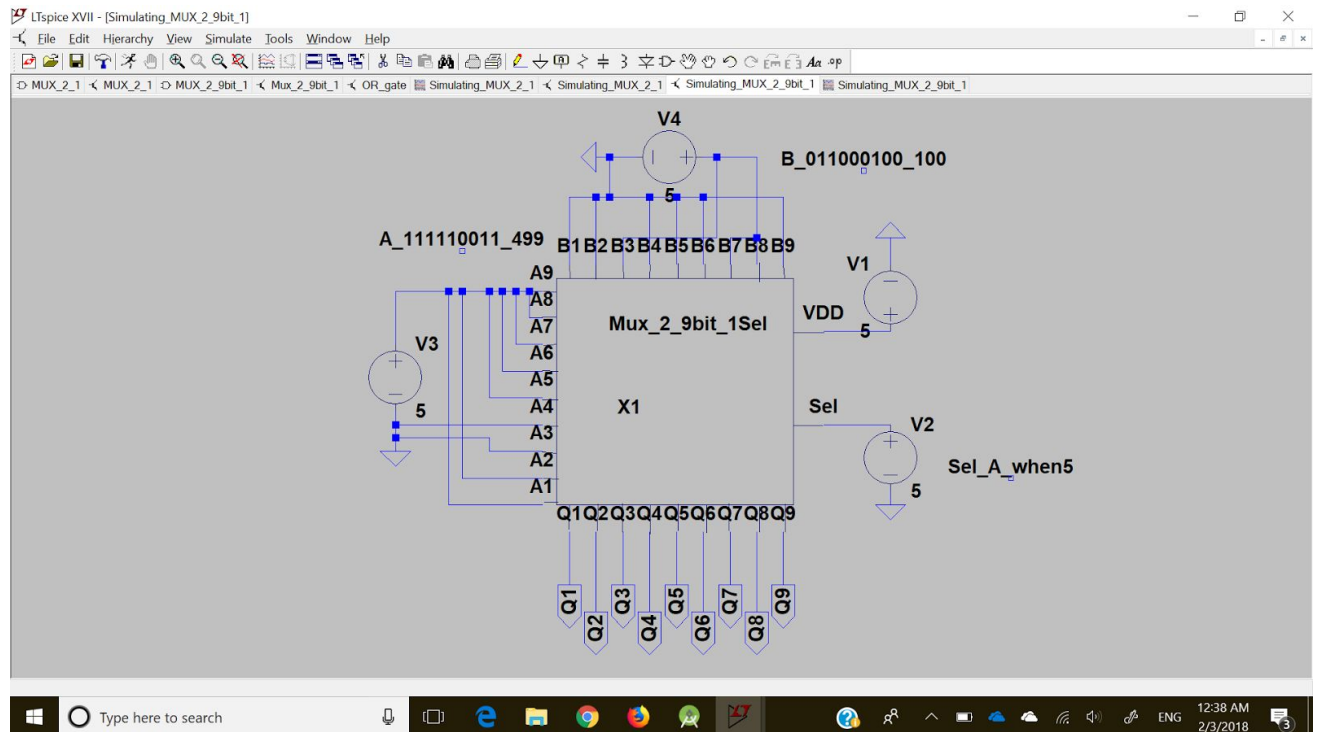


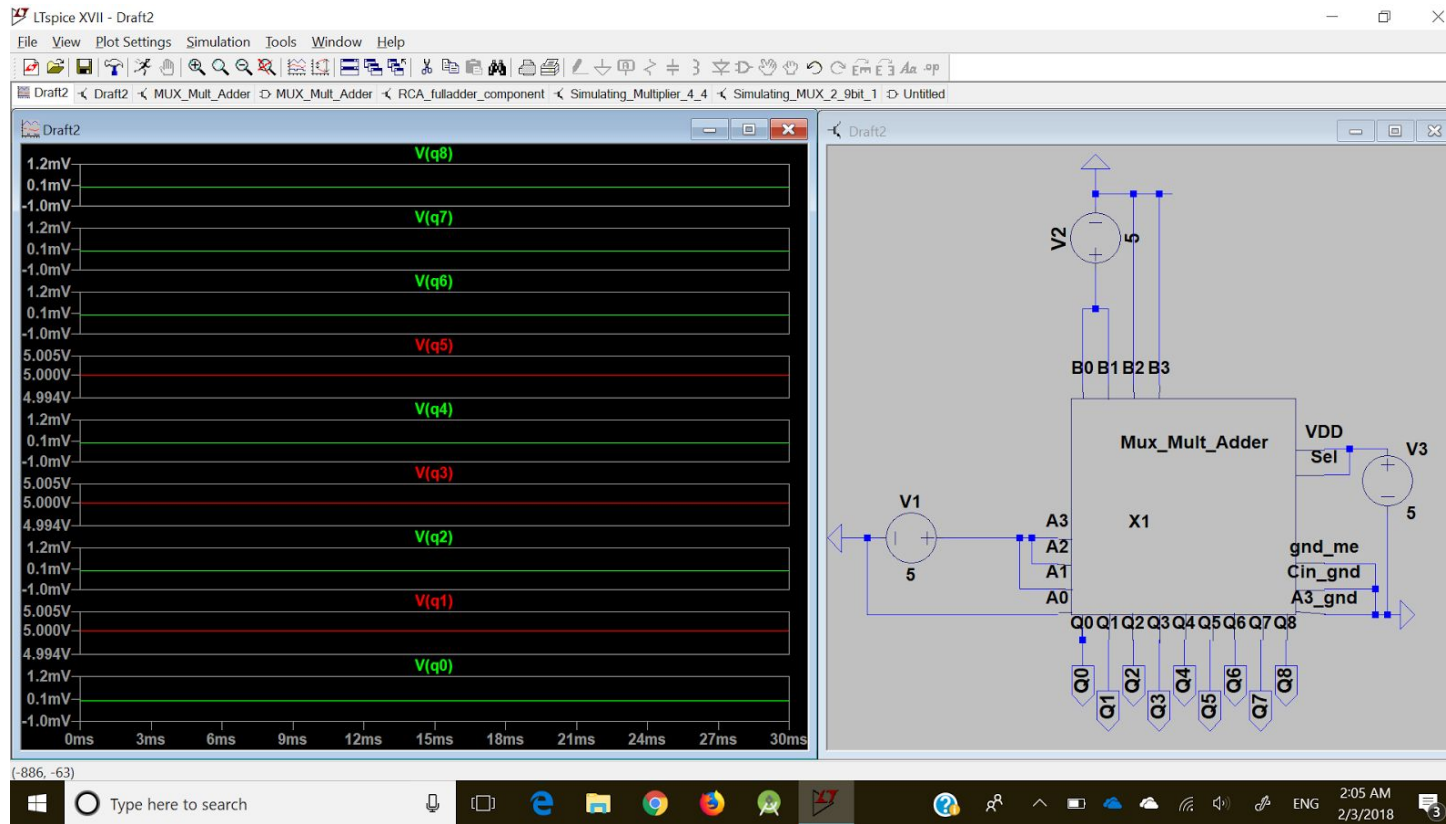9 bit Mux and Mux with Multiplier & Adder




5D) Pictured above is my 9bit 2input 1select MUX. I set the value of A to be 499 (111110011), B to be 100 (011000100) and Sel to be on. The Select then choose to make the output Q the A value 111110011 as shown.



5F)

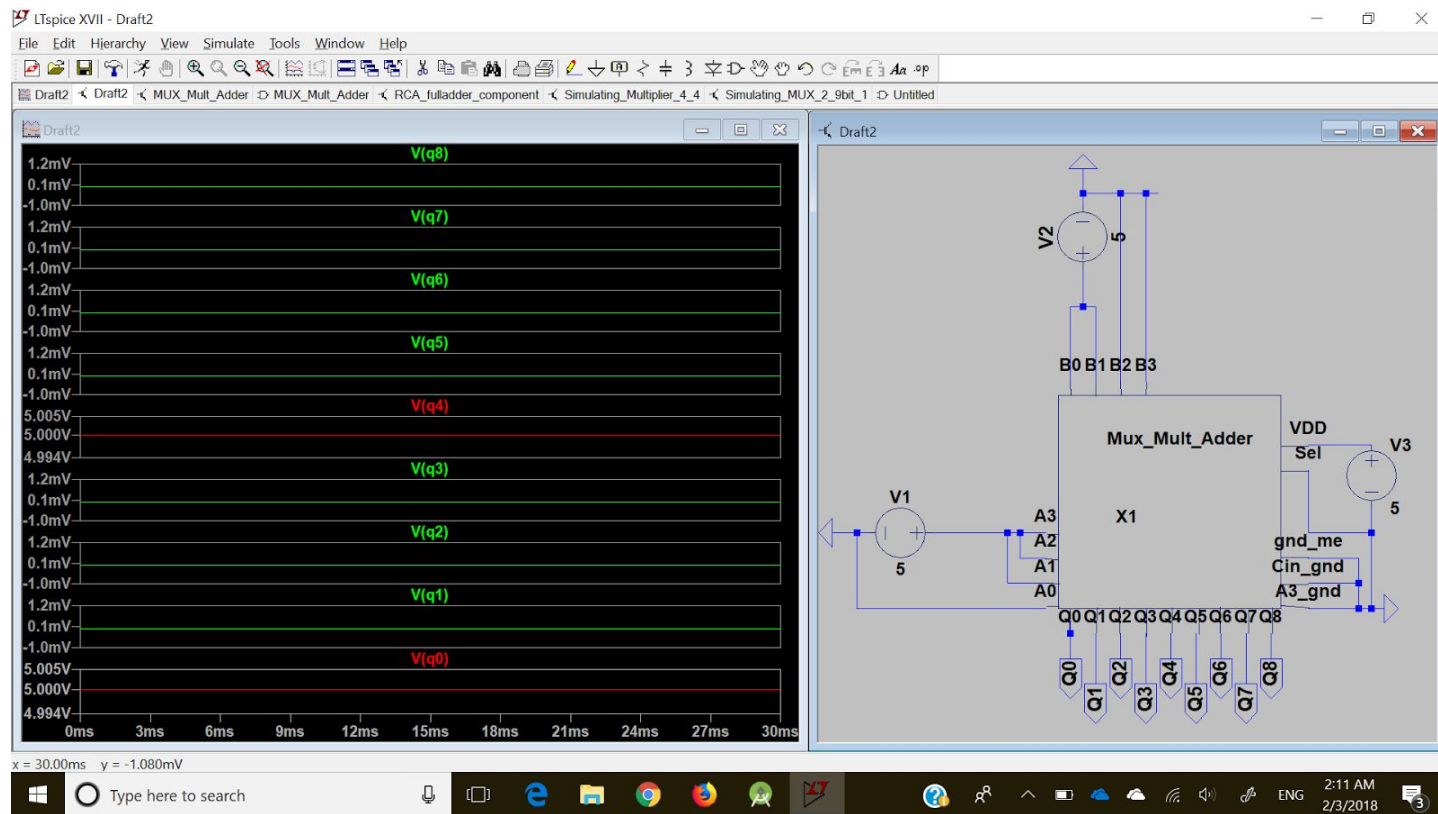Set A=1110 and B=0011 and Sel to "1" so the 9bit MUX chose the multiplier which results in $3 \times 14 = 42$ (000101010)



5F)

Set A=1110 and B=0011 and Sel to "0" so the 9bit MUX chose the adder which results in $3+14 = 17$ (000010001)