
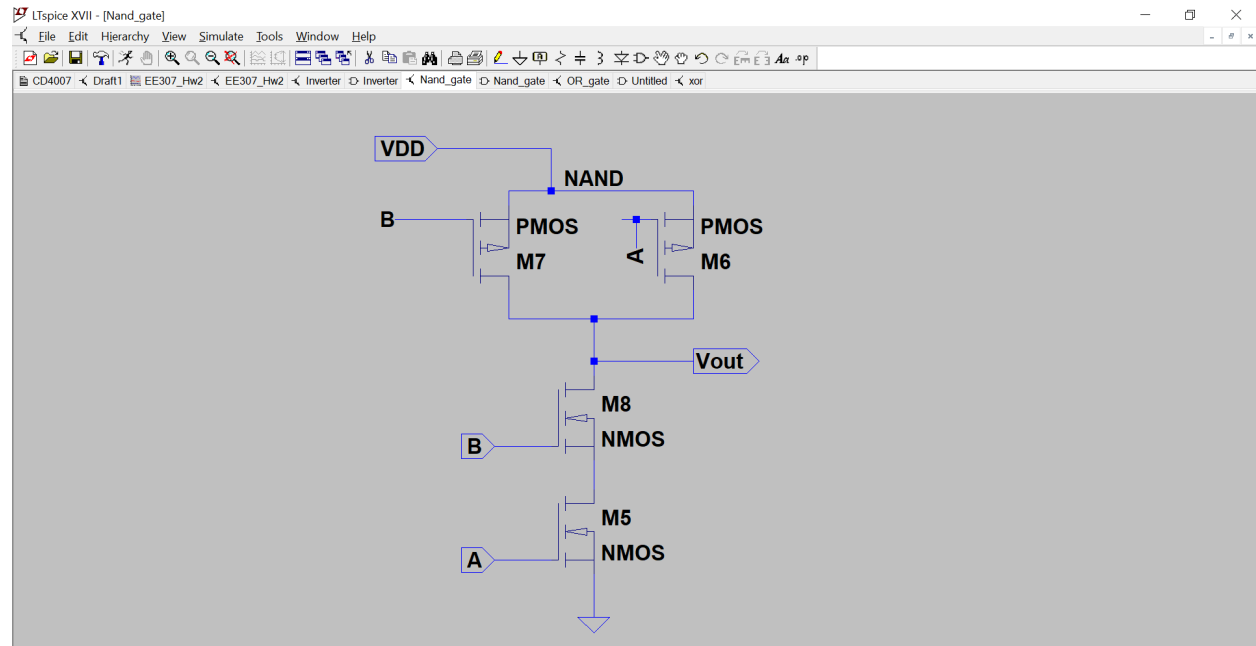


4. See page 3

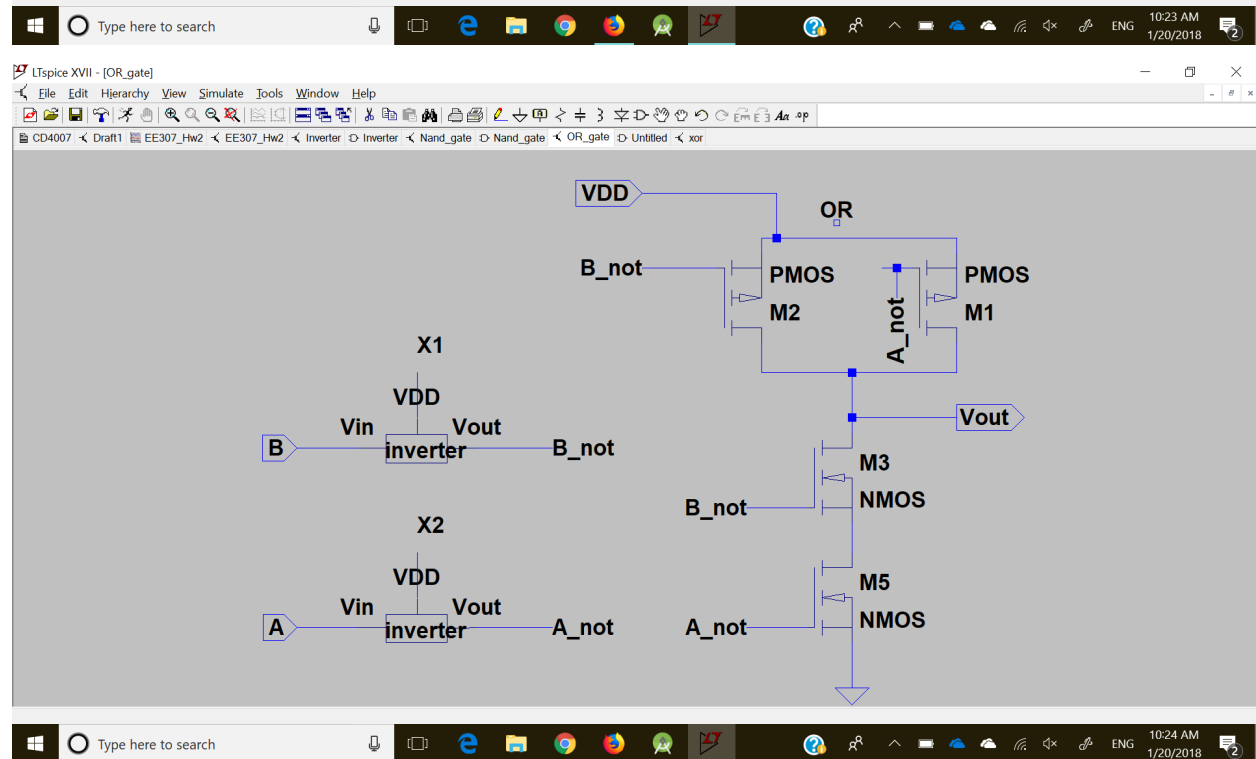


a.



b.

Inputs		Output Pull up network		Pull down network
A	B	Output		
0	0	0	OFF	ON
0	1	1	ON	OFF
1	0	1	ON	OFF
1	1	1	ON	OFF

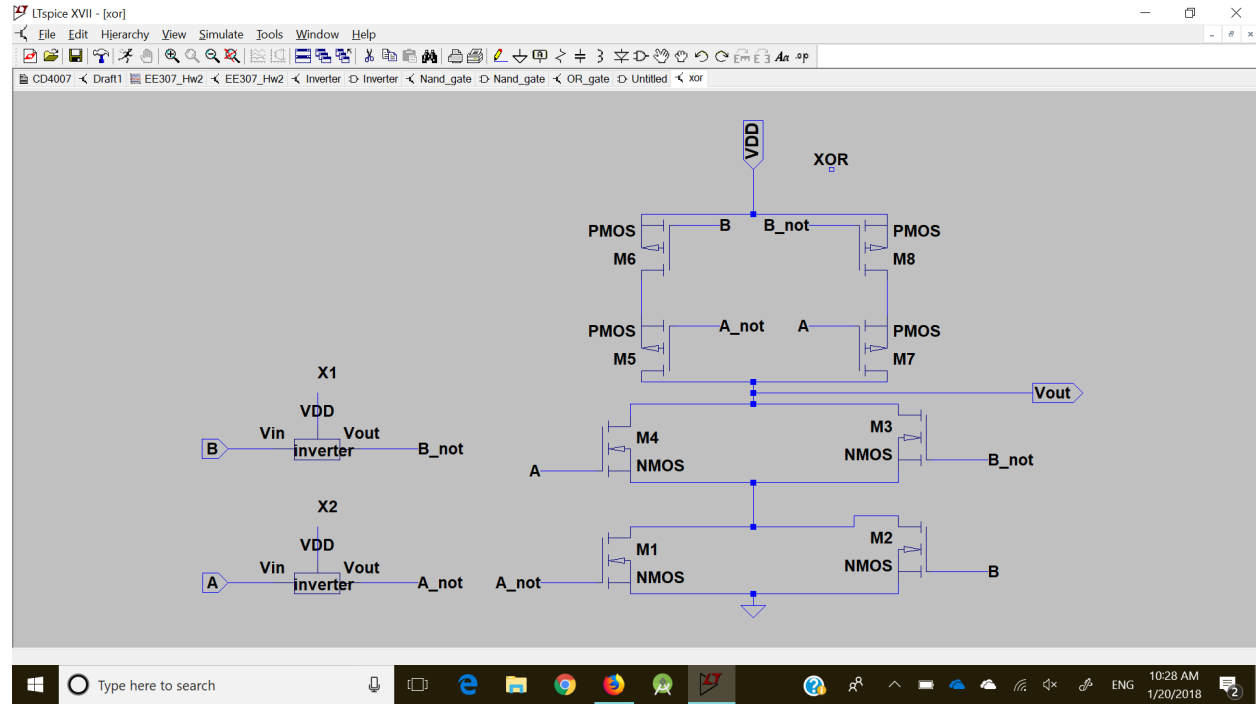

d.