

 


c.

 


d.

 



e.

Problem 6

 


6.

a.


The voltage pulses were chosen based off of:

A											
B											
AB	00	00	10	10	11	11	01	01	00	00	00

 
- b. Below is the simulation graph for my NAND gate, the Green is input A starting at 2ms and ending at 7ms.



 - c. Below is the simulation graph for my NAND gate; the Green is input B starting at 4ms and ending at 9ms.



 Below is the simulation graph for my NAND gate; the Blue is input A and the Green is input B.



A												
B												
AB	00	00	10	10	11	11	01	01	00	00	00	

In the simulation graph for my NAND gate, the output V_{out} is 5V from 0ms to approx. 4.5ms, 5V from approx. 6.5ms to 15ms and 0V from approx. 4.5ms to 6.5ms.

This is the expected output of a NAND gate because 4ms and 6ms correspond to when $AB = 11$.

