

2.

$t_R$  = rise time between 10% & 90% of swing

$$V_{out} = V_{max} (1 - e^{-t/RC})$$

$$V_{out} = V_{max} \times [1 - e^{-t/RC}] \quad \frac{V_{max}}{9}$$

$$\frac{1}{9} = e^{-t/RC}$$

$$-\ln(1/9) = -t/RC$$

$$t_R = RC \ln(9) = 2.2RC$$

b) high to low

$$V_{out} = V_{max} e^{-t/RC} = \frac{V_{max}}{9}$$

$$e^{-t/RC} = \frac{1}{9}$$

$$-t/RC = -\ln 9$$

$$t_F = \ln 9 RC = 2.2RC$$

collaborated w/ Regita & Tedmen Tran

Colleen Lam  
Feb 2, 2018  
HW4-EE357

$$c) \frac{V_{dd}}{2} = V_{dd} e^{-t/RC}$$

$$t_{PHL} = RC \ln 2 \quad t_{PLH} = RC \ln 2$$

$$t_P = \frac{1}{2} (t_{PHL} + t_{PLH})$$

$$t_P = RC \ln(2)$$

$$3. a) R_{ave} = \left( \frac{V_{DD}}{I_{DS V_{DD}}} \right) + \left( \frac{\frac{1}{2} V_{DD}}{I_{DS V_{DD}}} \right) \approx \left( \frac{3}{0.015} \right) + \left( \frac{1.5}{0.0125} \right) = 160 \Omega$$

$$b) R_{ave} = \left( \frac{V_{DD} \cdot \frac{3}{4}}{I_{DS V_{DD}}} \right) = \frac{(0.75 \cdot 3)}{14A \times 10^{-3}} = 181 \Omega$$

c) Active region for calculating  $R_{on}$  b/c that's when the circuit is on and transistor can be seen as resistor.

d) Using center point approximation

$$\frac{k'}{2} \frac{W}{L} = \frac{1}{1000} \frac{A}{V^2}, V_{TH} = 0.6 \quad V_{DD} = 5V$$

$$I_{DS} = \frac{1}{1000} \frac{A}{V^2} (5 - 0.6)^2 = 0.01936$$

$$\frac{5}{0.01936} = 193.618 \Omega$$



$$e) \left( \frac{V}{L} \right) \Rightarrow \left( \frac{40 \mu m}{2 \mu m} \right) (6.2) = 124 \Omega$$

$$f) (269.7) \left( \frac{5 \mu m}{2 \mu m} \right) = 10K$$

$$L = 76.71 \mu m$$

$$4. V_m = \frac{6V_{DD} - V_{DD}}{2} = 3V$$

a)

$$b) G = 2 - r'(V_m - V_2) \frac{1}{2 \lambda V_{DD}}$$

$$= 2 - 200 \frac{\mu A}{V^2} (3 - 0.5) \frac{1}{2(0.07)(0.00952)} = 9.445$$

$$I_D = \frac{\mu}{2} (V_{GS} - V_m)^2 (1 + \lambda V_{DD})$$

$$100 \mu A (3 - V_m)^2 (1 + (0.07)3) = 0.756 \mu m$$

$$c) V_{IL} \Rightarrow y = mx + b$$

$$V_{out}(V_m) = 9(1 + 9.445) = 31.33 = b$$

$$V_{max} = 6 = -9.945 V_m + 3(31.33) = V_{max} = 2.68$$

$$V_{min} = 0 = -9.945 V_m + 3(31.33) = 3.3176$$

$$d) V_{IL} = 2.68$$

$$V_{IH} = 3.3176$$

$$e) N_{ML} = 2.68 - 0 = 2.68V$$

$$f) N_{MH} = 6 - 3.3176 = 2.68$$



Colleen Lau  
Feb 2, 2018  
HW4 - EE307

5. Truth Table 2:1 MUX

a)

Sel	A	B	Q
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1



Sel	00	01	11	10
0	0	1	1	0
1	0	0	1	1

b)

$$Q = \overline{\text{Sel}} B + \text{Sel} A$$

c)

2:1 MUX

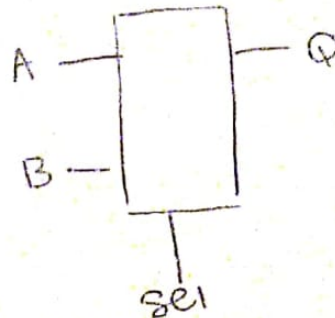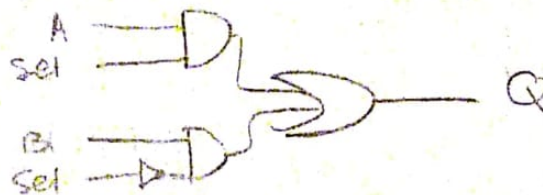

Mult-Adder-Mux


A when Sel = 1  
B when Sel = 0

\*  $\Rightarrow$  When Sel = 1  $\Rightarrow$  mult =  $3 \times 14 = 42$   
Sel = 0  $\Rightarrow$  adder =  $3 + 14 = 17$


101010

10001
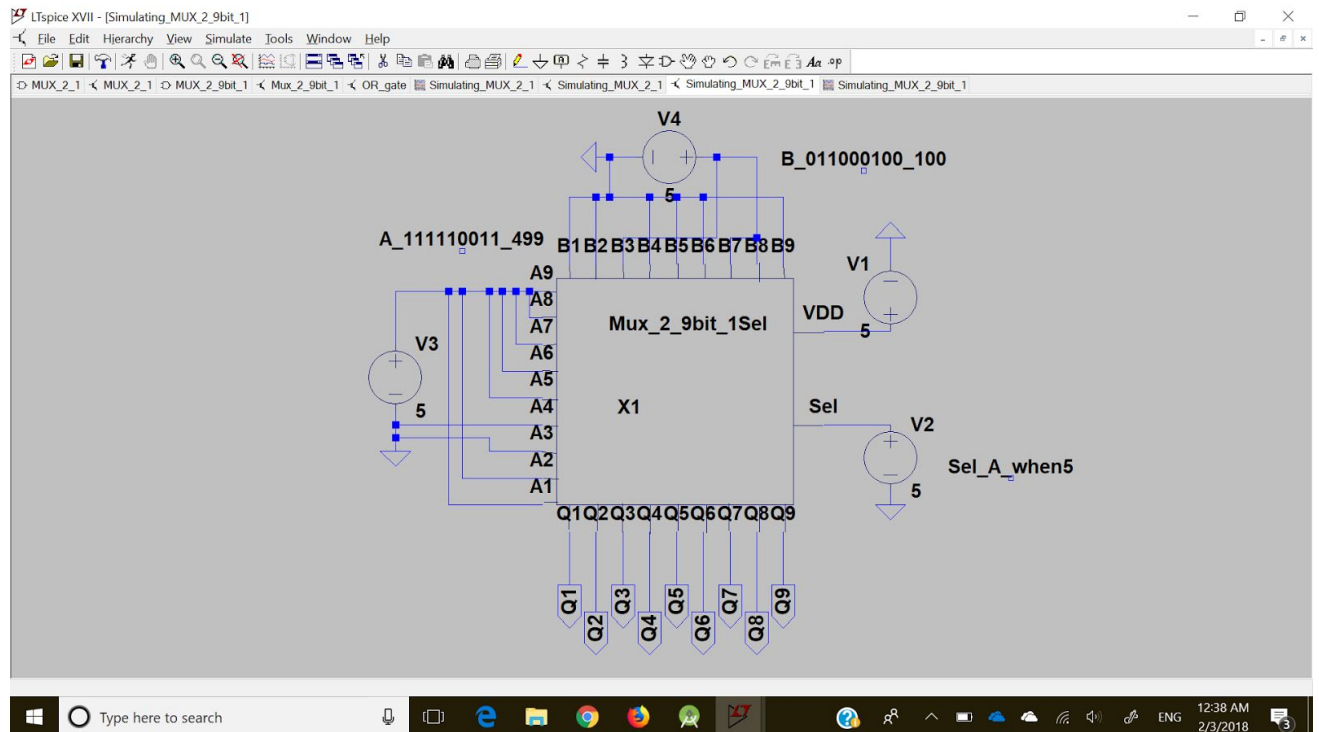
## 9 bit Mux and Mux with Multiplier & Adder




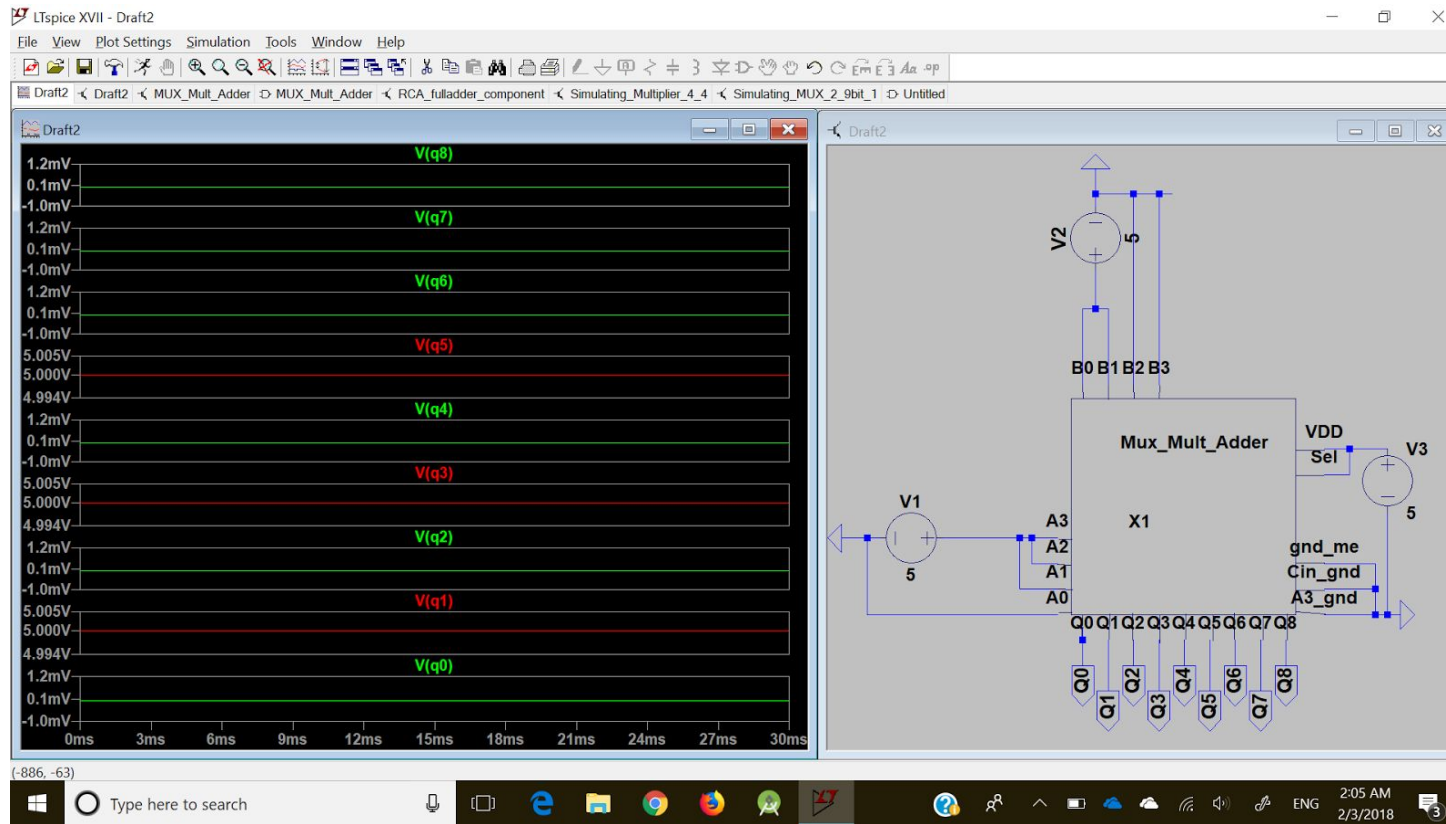5D) Pictured above is my 9bit 2input 1select MUX. I set the value of A to be 499 (111110011), B to be 100 (011000100) and Sel to be on. The Select then choose to make the output Q the A value 111110011 as shown.



5F)

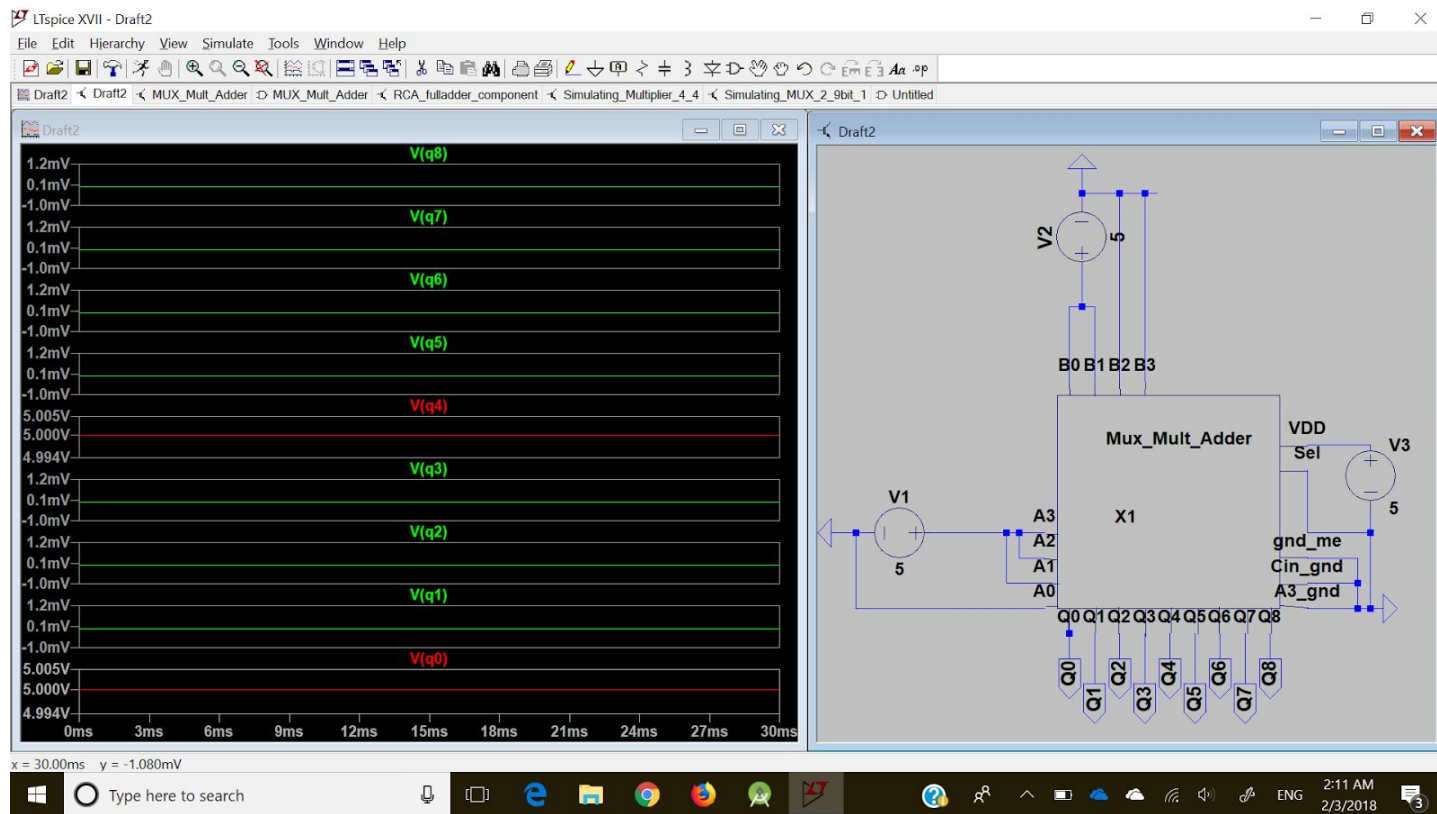Set A=1110 and B=0011 and Sel to "1" so the 9bit MUX chose the multiplier which results in  $3 \times 14 = 42$  (000101010)



5F)

Set A=1110 and B=0011 and Sel to "0" so the 9bit MUX chose the adder which results in  $3+14 = 17$  (000010001)